

Code No: 151AG

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech I Year I Semester Examinations, September/October - 2021

BASIC ELECTRICAL ENGINEERING

(Common to EEE, CSE, IT, CSIT, ITE, CE(SE), CSE(CS), CSE(DS), CSE(Networks))

Time: 3 Hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

1. Find the current supplied by 10V battery for the following network shown in figure 1. [15]

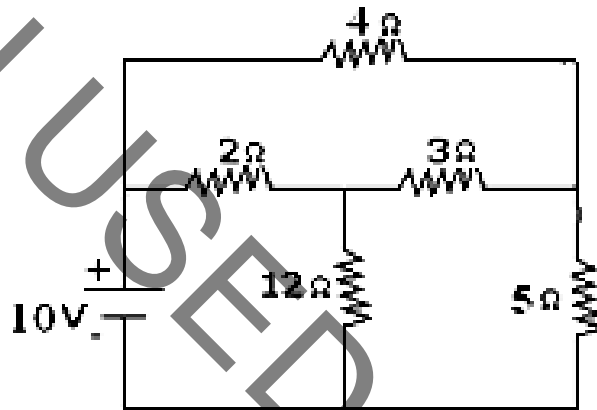


Figure: 1

2. By using Norton's theorem, determine the current through 5Ω resistor for the circuit shown in figure 2. [15]

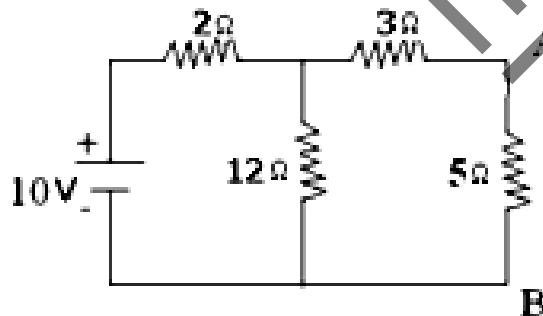


Figure: 2

- 3.a) Derive the expression for the average value and form factor of a sinusoidal waveform.
b) Find the RMS voltage of the signal shown in figure 3. [7+8]

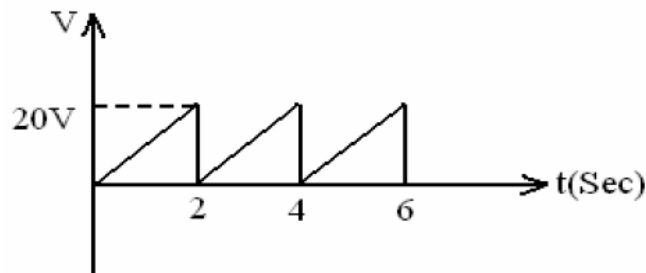


Figure: 3

- 4.a) What is series resonance? Explain with respect to series R-L-C circuit connected across sinusoidal voltage source.
- b) Show that the resonant frequency ω_0 of an RLC series resonant circuit is the geometric mean of ω_1 and ω_2 , the lower and upper half power frequencies respectively. [7+8]
- 5.a) Derive an emf equation of a single phase transformer.
- b) Explain about hysteresis and eddy current losses occur in a transformer. [8+7]
- 6.a) Explain the operation of a transformer under no load and load conditions with the help of phasor diagrams.
- b) Explain different poly phase transformers connections. [8+7]
- 7.a) Give the constructional details of 3-phase Induction motor.
- b) Explain the torque speed characteristics of 3-phase Induction motor. [8+7]
- 8.a) Differentiate between MCB and MCCB.
- b) Explain the different types of batteries in detail. [6+9]

---ooOoo---

SEPTEMBER-2021