

Code No: 181AH

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech I Year I Semester Examinations, March/April - 2023

ELECTRICAL CIRCUIT ANALYSIS –I

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 60

Note: This question paper contains two parts A and B.i) **Part- A** for 10 marks, ii) **Part - B** for 50 marks.


- Part-A is a compulsory question which consists of ten sub-questions from all units carrying equal marks.
- Part-B consists of **ten questions** (numbered from 2 to 11) **carrying 10 marks each**. From each unit, there are two questions and the student should answer one of them. Hence, the student should answer five questions from Part-B.

PART - A**(10 Marks)**

- 1.a) What are the independent sources? [1]
- b) Define super mesh. [1]
- c) Write the relations between real power, reactive power and apparent power. [1]
- d) Define Form factor of a sinusoidal waveform. [1]
- e) What are the limitations of maximum power transfer theorem? [1]
- f) State Milliman's theorem. [1]
- g) What do you mean by 3-phase balance circuits? [1]
- h) What is phase sequence? [1]
- i) What is meant by coefficient of coupling? [1]
- j) Define incidence matrix. [1]

PART - B**(50 Marks)**

- 2.a) Find the current through $20\ \Omega$ resistor using Kirchoff's laws(Figure 1).

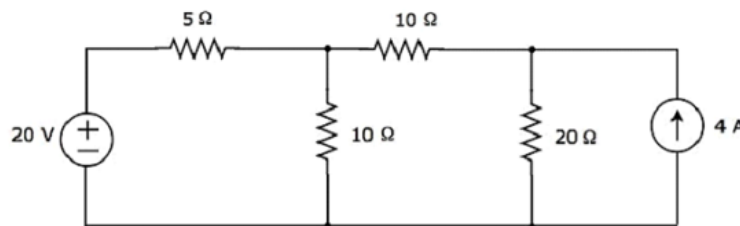**Figure 1**

- b) Find the current through $10\ \Omega$ resistor using Kirchoff's laws(Figure 2). [5+5]

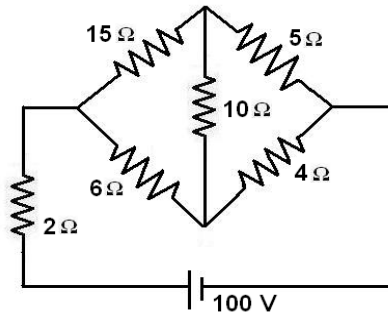


Figure 2

OR

- 3.a) Obtain the delta-star conversion equations with examples.
 b) By using the nodal analysis, determine various node voltages in the following circuit(Figure 3). [4+6]

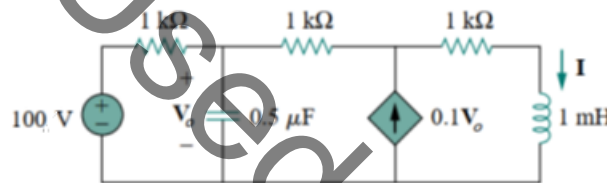


Figure 3

- 4.a) Draw and discuss phasor diagram and impedance triangle of a series RLC circuit. Also find out the circuit impedance, current and powers with various cases.
 b) A resistance of 50 ohms is connected in series with a capacitor of 50 micro farad to a supply at 220 V, 50 Hz. Find i) impedance ii) current iii) power factor and iv) power. [6+4]

OR

- 5.a) For the circuit shown in figure 4, find the current I drawn from the source, I_1 and I_2 .

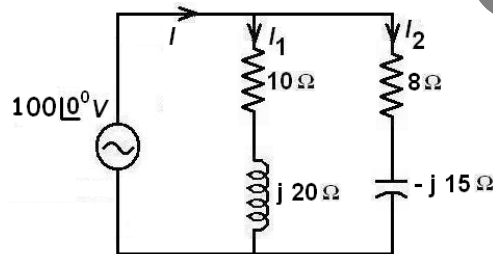


Figure 4

- b) Find the resonant frequency and Q factor for series RLC circuit consists of a resistance of $1000\ \Omega$, inductance of 100mH and a capacitance of 10pF. If the voltage of 100V is applied across the circuit. [6+4]

6.a) Using Superposition theorem, find the current in $2\ \Omega$ (Figure 5).

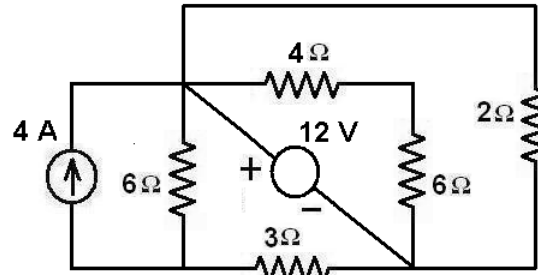


Figure 5

b) Determine maximum power transfer to $(4 - j3)\ \Omega$ branch (Figure 6).

[5+5]

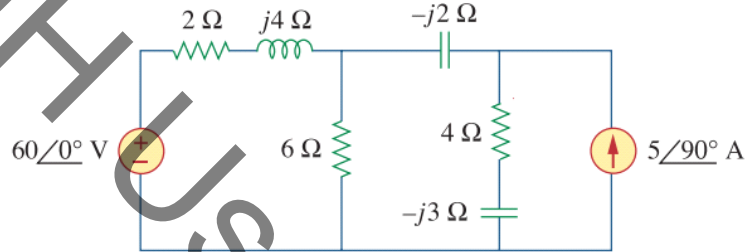


Figure 6

OR

7. State and explain reciprocity and compensation theorems with examples. [10]

8. Derive the relationship between phase quantities and line quantities in a 3-phase balanced star connected system and Draw phasor diagram showing voltages and currents. [10]

OR

9.a) The two-watt meter readings in a 3 - phase power measurement are 800 W and 400 W. The latter reading is being obtained after the reversal of current coil. Calculate the total power and power factor of the load.

b) Three identical impedances of $(3+j4)$ ohm are connected in delta. Find an equivalent star network such that the line current is the same when connected to the same supply. [5+5]

10.a) Two coils A and B having turns 100 and 1000 respectively are wound side by side on closed circuit coil of cross-section $8\ \text{cm}^2$ and mean length 80 cm. The relative permeability of iron is 900. Calculate the mutual inductance between the coils.

b) Two coupled coils with $L_1=0.01\ \text{H}$ and $L_2=0.04\ \text{H}$ and $K=0.6$ are connected in four different ways. Find the equivalent inductance if coils are connected in (i) series aiding (ii) series opposing (iii) parallel aiding (iv) parallel opposing. [5+5]

OR

11.a) Draw the graph of the network shown in below figure 7 below

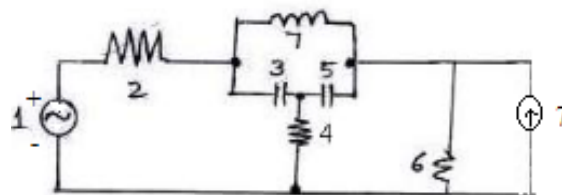


Figure 7

b) Explain the procedure for obtaining fundamental tie-set matrix of given network. [5+5]