

Code No: 181AM

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech I Year I Semester Examinations, January/February - 2024

FUNDAMENTALS OF ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to BT, PCE)

Time: 3 Hours

Max. Marks: 60

Note: This question paper contains two parts A and B.

i) **Part - A** for 10 marks, ii) **Part - B** for 50 marks.

- Part-A is a compulsory question which consists of ten sub-questions from all units carrying equal marks.
- Part-B consists of **ten questions** (numbered from 2 to 11) **carrying 10 marks each**. From each unit, there are two questions and the student should answer one of them. Hence, the student should answer five questions from Part-B.

PART - A**(10 Marks)**

- Write the relationship between voltage and current in an inductor. [1]
- What is a mesh? [1]
- Define peak factor. [1]
- What is meant by phase difference? [1]
- What a commutator does in d.c generator? [1]
- What are the parts of an alternator? [1]
- How a diode behaves in reverse bias? [1]
- What is an ideal diode? [1]
- How many junctions are there in BJT? [1]
- What are the types of BJT? [1]

PART - B**(50 Marks)**

- What are the types of electrical sources? Explain.
- Using mesh analysis, find the current 'I' in the circuit below figure 1. [5+5]

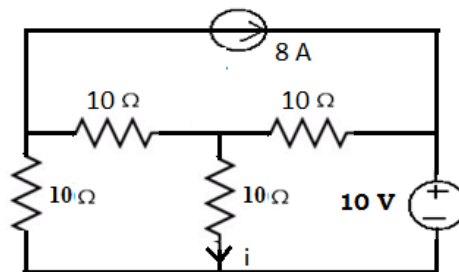


Figure 1

OR

- 3.a) What are Kirchoff's laws? Explain with examples.
 b) Using nodal analysis, find the current 'I' in the circuit below figure 2. [5+5]

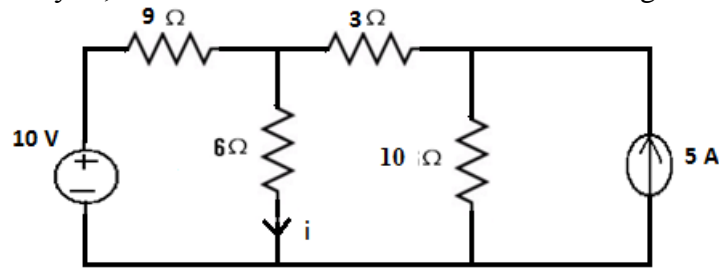


Figure 2

- 4.a) Derive the expression for the steady state current in series RL circuit with sinusoidal voltage source.
 b) The current flowing through a circuit is $10\sqrt{30}^0 A$ when a voltage of $200\sqrt{-15}^0 V$ is applied. Calculate the components of the circuit if frequency of the supply is 50 Hz. [5+5]

OR

- 5.a) What is the average value of sinusoidal voltage source? Derive it.
 b) Determine the voltage across resistor and capacitor in the circuit below figure 3. [5+5]

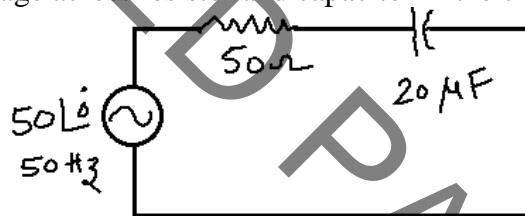


Figure 3

- 6.a) Explain the constructional features of DC machines in detail.
 b) How 3-φ induction motor works? Explain. [5+5]

OR

- 7.a) How EMF is induced in DC generator? Explain.
 b) Explain the principle of operation of transformer. [5+5]

- 8.a) How a PN Junction diode works? Explain.
 b) Explain the working of half wave rectifier? [5+5]

OR

- 9.a) Draw the V-I characteristics of PN junction diode and explain.
 b) Explain the working of full wave bridge rectifier? [5+5]

- 10.a) How a BJT works? Explain in detail.
 b) Explain the CB configuration of BJT with the help of neat circuit diagram. [5+5]

OR

- 11.a) Explain about the doping level and size of the layers of BJT.
 b) Discuss about the differences between different configurations of BJT. [5+5]