

Code No: 182AC

R22

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech I Year II Semester Examinations, September - 2023

BASIC ELECTRICAL ENGINEERING

(Common to ECE, EIE, CSE (AI&ML), CSE(IOT), AI&DS, AI&ML)

Time: 3 Hours

Max. Marks: 60

Note: This question paper contains two parts A and B.

i) Part- A for 10 marks, ii) Part - B for 50 marks.

- Part-A is a compulsory question which consists of ten sub-questions from all units carrying equal marks.
- Part-B consists of **ten questions** (numbered from 2 to 11) **carrying 10 marks each**. From each unit, there are two questions and the student should answer one of them. Hence, the student should answer five questions from Part-B.

**PART- A**


(10 Marks)

- 1.a) Draw the equivalent circuit of Norton's theorem. [1]
- b) Write the time constant of RC circuit. [1]
- c) Define Peak factor. [1]
- d) Write the line voltage and phase voltage relation in star connections. [1]
- e) What is ideal transformer? [1]
- f) The efficiency of the transformer is high compared to other electrical machines. Give the reason. [1]
- g) What are the parts of synchronous generator? [1]
- h) Define Slip. [1]
- i) Differentiate ELCB and MCCB. [1]
- j) Differentiate fuse and earthing. [1]

**PART - B**

(50 Marks)

- 2.a) Find the power supplied by the 2V source in the circuit shown below. (Figure 1)

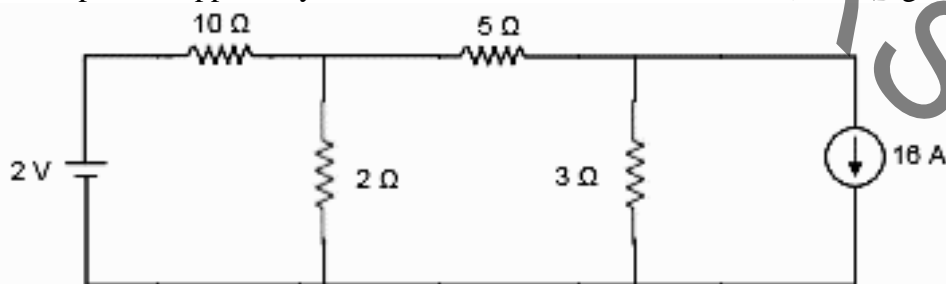

**Figure 1**

- b) A capacitor in an RC circuit with  $R = 25 \text{ Ohm}$  and  $C = 50 \text{ micro Fared}$  is being charged with initial zero voltage. What is the time taken for the capacitor voltage to reach 40 percentage of its steady state value? [5+5]

**OR**

- 3.a) Determine the current  $I$  and  $I_0$  for the following circuit.(Figure 2)

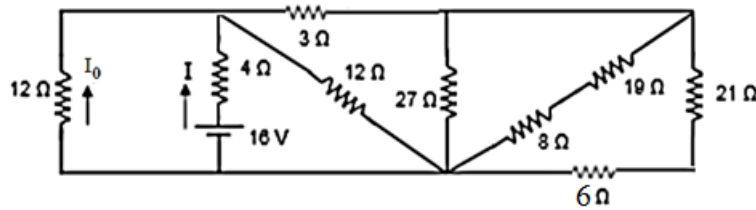


Figure 2

- b) Calculate the power consumed by the 2 Ohm resistor.(Figure 3) [5+5]

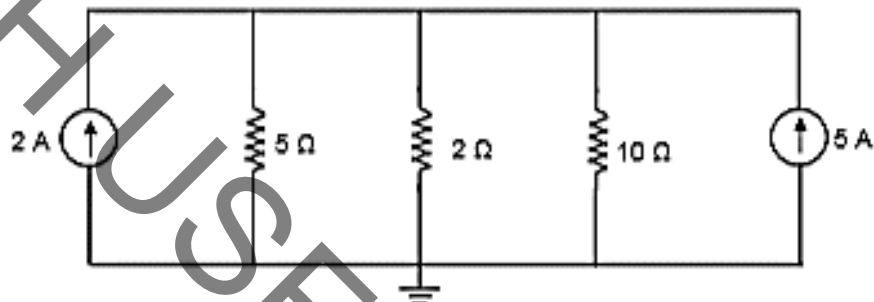


Figure 3

4. A balanced three phase load connected in star consists of  $(6 + j8)$  ohms impedance in each phase. It is connected to a three phase supply of 400 V, 50 Hz. Find:  
 a) Magnitude of phase current and line current  
 b) Per phase power and  
 c) Total power [10]

OR

- 5.a) A variable frequency 200 V supply is connected to a RLC series circuit with  $R = 10$  ohms and  $L = 10$  milli henry and  $C = 1$  micro Fared. For resonance condition, calculate the current and the voltages across R. Take the supply voltage as reference. [6+4]  
 b) Obtain the form factor of sinusoidal waveform.

- 6.a) Explain the working principle of Auto transformer.  
 b) In a 25 KVA, 2000/200 V transformer, the constant and variable losses are 350 W and 400 W respectively. Calculate the efficiency on u.p.f at full load and half load. [5+5]

OR

- 7.a) Explain hysteresis and eddy current losses in a transformer.  
 b) The percentage resistance and reactance of a transformer are 2 % and 4 % respectively. Find the approximate regulation on full load at unity power factor. [5+5]

- 8.a) Explain the working principle of three phase induction motor.  
 b) A 6 pole lap wound D.C. Generator has 720 conductors, a flux of 40 m Wb per pole is driven at 400 RPM. Find the generated e.m.f. [5+5]

OR

9.a) A 4 pole lap wound d.c shunt generator supplies to 50 lamps of 100 watts, 200V each. The field and armature resistance are 50 Ohms and 0.2 Ohms respectively. Allowing a brush drop of 1 V each brush, calculate the generated e.m.f.

b) Explain the significance of Torque slip characteristics of three phase induction motor.

[5+5]

10.a) Write short notes on SFU and MCB.

b) Explain the various types of cables used in distribution of power.

[5+5]

**OR**

11.a) Explain the various types of wires used in electrical installations.

b) Brief about the characteristics of batteries.

[5+5]

---ooOoo---

UNIVERSITY USED PAPERS-2023