

Code No: 154AW

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B. Tech II Year II Semester Examinations, August/September - 2022****ELECTRONIC CIRCUIT ANALYSIS****(Electronics and Computer Engineering)****Time: 3 hours****Max. Marks: 75**

**Answer any five questions**  
**All questions carry equal marks**

- - -

- 1.a) Derive the components of the Hybrid -  $\pi$  model in terms of h parameters in CE Configuration.
- b) Draw the circuit for CASCODE Amplifier. Explain its working, and how it is useful at high frequency? [9+6]
- 2.a) Draw and derive the expression for input impedance and current gain of Darlington amplifier.
- b) Explain different coupling schemes used in amplifiers. [9+6]
- 3.a) Explain the characteristics of negative feedback amplifier.
- b) Derive the expressions for the input and output resistances of current series feedback amplifier. [7+8]
- 4.a) Explain the method of analysis of voltage series amplifier.
- b) An amplifier have a voltage gain of 200, input resistance 10 k $\Omega$  and output resistance of 50k $\Omega$ . If 2% of input voltage is feedback to the input in series opposition than, calculate modified values of gain, input and output resistances. [8+7]
- 5.a) Draw the circuit diagram for crystal oscillator and explain its operation.
- b) Derive the frequency of oscillation of Hartley oscillator. [8+7]
- 6.a) Derive an expression for the frequency of oscillation of a RC phase shift oscillator. Determine the min  $h_{fe}$  for the transistor to sustain oscillations.
- b) In a Colpitts oscillator  $C_1 = 0.001 \mu\text{F}$  and  $C_2 = 0.01 \mu\text{F}$  and  $L = 5 \mu\text{H}$ . Calculate:  
i) Frequency of oscillations. ii) If 'L' is doubled, find the new frequency. [9+6]
- 7.a) What is a stagger tuned amplifier? Explain its advantages and disadvantages.
- b) How is the bandwidth of tuned amplifier improved? Draw such a circuit and explain its working. [7+8]
- 8.a) Draw the circuit diagram of Boot strap time base generator and explain its operation in detail.
- b) Sketch the circuit diagram of Schmitt trigger and explain its operation. [8+7]