

Code No: S9505

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, November/December - 2017

NETWORK THEORY

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Explain the procedure and necessary formulas for star to delta and delta to star conversion of 3 ϕ balanced loads.
- b) The balanced load in figure 1 shown below is fed by a balanced three-phase system having $V_{ab} = 230\angle 0^\circ$ V rms and positive phase sequence. Find the reading of each wattmeter and the total power drawn by the load. [7+8]

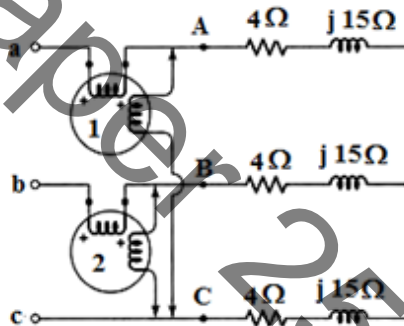


Figure 1

- 2.a) A simple RL circuit as shown in below figure 2, the switch is opened at time $t = 0$ sec. Find the current response $i_L(t)$ valid for time $t > 0$ sec.

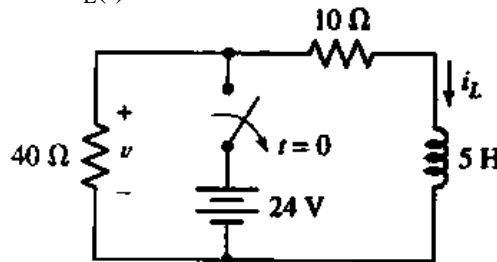


Figure 2

- b) Find the capacitor voltage $v_C(t)$ and the current $i(t)$ in 200 Ω resistor, valid for all time, in the circuit shown in below figure 3. [7+8]

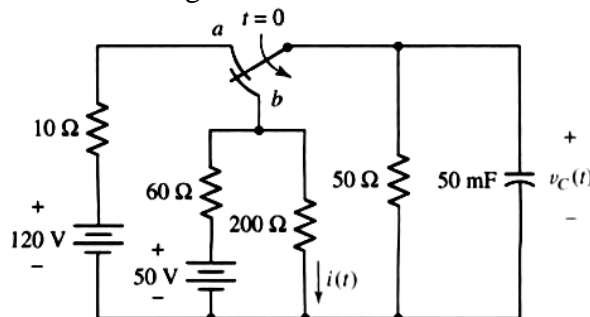


Figure 3

3. Find the current i_L in the circuit shown in figure 4 below using Laplace Transforms. [15]

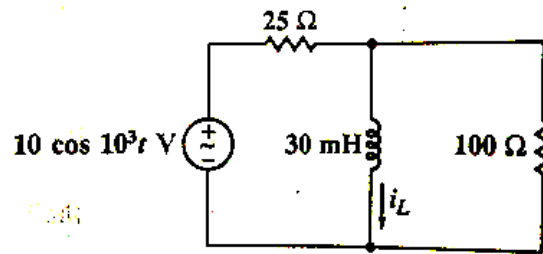


Figure 4

- 4.a) What do you understand by Network Functions? Define any four basic Network Functions.
 b) For the two-port network shown in figure 5 below, find (i) Voltage transfer function and (ii) Transfer impedance function. [7+8]

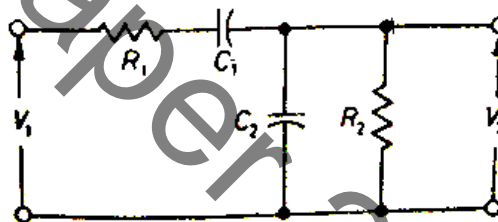


Figure 5

- 5.a) Define Z, Y and Transmission parameters of a Two-Port network and give their interrelationships between the parameters.
 b) Determine h_{21} of the network shown in figure 6 below. [7+8]

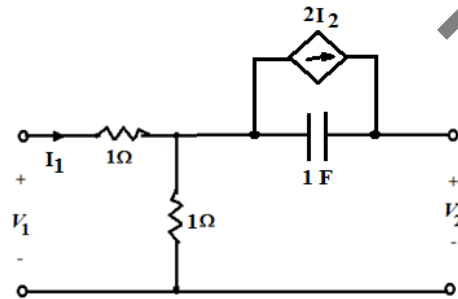


Figure 6

6. Determine the driving point impedance of the network shown in figure 7 below, as seen from terminals 1, 1' given that N_1 and N_2 are identical. Each of the two parts is characterised by $Z_{oc} = \begin{bmatrix} 2 & 1 \\ 1 & 1 \end{bmatrix}$. [15]

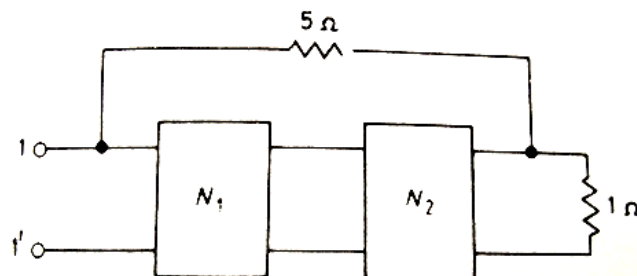


Figure 7

7. Explain the design procedure of constant K - low pass filter. [15]

8.a) Specify the types of symmetry present in the waveform of figure 8 shown below.



Figure 8

b) A function $f(t)$ has both odd and half-wave symmetry. The period is 8 ms. It is also known that $f(t) = 10^3 t$, $0 < t < 1$ ms, and $f(t) = 0$, $1 < t < 2$ ms. Find values for b_n , $1 \leq n \leq 5$. [7+8]

---ooOoo---