

Code No: S9504

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, November/December - 2017

ELECTRONIC CIRCUITS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Describe the methods of determination of h-parameters from its static Input and output characteristics.
- b) Draw and explain the h-parameter equivalent circuit of a transistor in CC configuration. Derive the expressions for input impedance, output impedance. [7+8]
- 2.a) Assume the effect of coupling capacitors on the low frequency response of BJT amplifier.
- b) Explain the analysis of low frequency FET amplifier. [7+8]
- 3.a) Explain voltage series and shunt feedback amplifier with an example.
- b) Describe the characteristics of negative feedback amplifier. [8+7]
4. Derive the expression and characteristics of oscillator
- a) RC Phase shift
- b) Hartley. [8+7]
- 5.a) Derive an expression for the upper cut-off frequency of a low pass circuit.
- b) Explain the operation of the transformer coupled class A audio power amplifier and derive the maximum value of efficiency used in audio power amplifier. [7+8]
- 6.a) Explain the operation of shunt negative clipper with circuit diagram and input- output waveforms.
- b) Explain the operation of positive clamper with circuit diagram and input – output waveforms. [8+7]
- 7.a) Explain details about the switching characteristics on PN diode with neat Sketch.
- b) Explain details about the switching characteristics of transistor with neat Sketch. [7+8]
- 8.a) What is monostable multivibrator? Explain with the help of a neat circuit diagram the principle of operation of a monostable multi and derive an expression for pulse width.
- b) Derive an expression for the period of oscillations of astable multivibrator. [8+7]

---ooOoo---