

RA

Code No: 155SR

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, January/February - 2023

ANALOG ELECTRONICS
(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

- Note:** i) Question paper consists of Part A, Part B.
ii) Part A is compulsory, which carries 25 marks. In Part A, Answer all questions.
iii) In Part B, Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART – A

(25 Marks)

- 1.a) Explain about Zener break down. [2]
- b) Write a short note on small signal analysis of transistor. [3]
- c) Define trans conductance of FET. [2]
- d) How FET works as switch? [3]
- e) What are the drawbacks of transformer coupled power amplifiers? [2]
- f) Classify power Amplifiers. [3]
- g) What is the effect of negative feedback on bandwidth? [2]
- h) List the four feedback topologies and draw its basic block diagrams. [3]
- i) Define the input offset current. [2]
- j) Draw and label the Ideal op-amp. [3]

PART – B

(50 Marks)

- 2.a) How the diode used for clipping? Draw and explain two level clipping circuit.
 - b) Explain about the half-wave rectifier without filters. [5+5]
- OR**
3. Explain BJT common-base configuration, and sketch a circuit for determining CB characteristics. [10]
- 4.a) Draw and explain the small signal equivalent circuit of MOSFET.
 - b) Discuss the MOSFET characteristics in depletion mode. [5+5]
- OR**
- 5.a) Compare the performance of BJT and FET amplifiers.
 - b) Draw and explain the CS amplifier with current source load. Derive an expression for A_v . [5+5]

6.a) Derive the expression for maximum conversion efficiency for a simple series fed Class A power amplifier.

b) A push pull amplifier utilizes a transformer whose primary has a total of 160 turns and whose secondary has 40 turns. It must be capable of delivering 40W to an 8Ω load under maximum power conditions. What is the minimum possible value of V_{CC} ? [5+5]

OR

7.a) Briefly explain the distortion in power-amplifier and Thermal stability.

b) Design a class B power amplifiers to deliver 25W to a load resistor $R_L=8$ ohms, using transformer coupling. $V_m=V_{CC}=25V$. Assume necessary data. [5+5]

8.a) Draw the voltage shunt feedback amplifier circuit and explain them briefly.

b) What are the characteristics of an amplifier that are modified by negative feedback? [5+5]

OR

9. Starting from the description of a generalized Oscillator, derive the expression for frequency of Oscillation in a Colpitts Oscillator. [10]

10.a) Draw the current to voltage converter circuit using op-amp.

b) Explain and draw the circuit of a voltage regulator. [5+5]

OR

11. Explain the term Slew rate and how it effects the frequency response of op-amp? Derive the expression for slew rate. [10]

---ooOoo---