

Code No: 155SJ

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, March - 2021

LINEAR AND DIGITAL IC APPLICATIONS

(Electronics and Instrumentation Engineering)

Time: 3 hours

Max. Marks: 75

Answer any five questions  
All questions carry equal marks

- - -

- 1.a) Draw the basic circuit diagram of an Op-amp differentiator and explain its operation and stability.
- b) Mention the characteristics of an ideal Op-Amp. [10+5]
- 2.a) Explain the features of 723 voltage regulators with a neat diagram.
- b) Draw non-converting op-amp circuit. And explain its working. [10+5]
- 3.a) Design a narrow bandpass filter with a centre frequency  $f_c = 1\text{KHz}$ ,  $Q = 5$ ,  $A_f = 8$ . Change the centre frequency to  $2\text{KHz}$ , keeping  $A_f$  and  $B_w$  constant.
- b) Compare passive and active filters. [10+5]
- 4.a) Explain the operation of 555 IC with the help of functional diagram.
- b) What do you mean by quantization error in an A/D converter? [10+5]
5. Explain the operation of dual slope ADC. [15]
- 6.a) With a neat sketch explain the operation of an n-bit Weighted Resistor DAC and obtain expression for its output.
- b) What are the limitations of weighted resistor type D/A converter? [10+5]
- 7.a) Draw and explain the operation of priority encoder.
- b) Design a full adder with minimum number of NAND gates. [8+7]
- 8.a) Draw the circuit diagram of a negative edge triggered J-K Flip-Flop with active high present and clear and explain its operation with the help of truth table.
- b) Differentiate between ripple counter and synchronous counter? Design a 4-bit counter in both modes and estimate the propagation delay. [8+7]

---ooOoo---